

Lecture 2 – measurement in physics


- Why electronic measurement is so useful.
- Input and output impedances. (Measuring with Oscilloscopes)
- Ideal operational amplifiers (op-amp). (Amplifying)
- Non-ideal behavior of op-amps.

The oscilloscope as a “perfect” measurement tool


- Probably the most important measuring device in laboratory physics as many transducers produce a voltage output. It's essential to know how to use one and what its limitations are.
- Oscilloscopes measure $V(t)$ rather well. At up to few 100 MHz, and at least 500× higher if you are willing to pay money.
- And critically, they meet point 1 – they don't affect what they're measuring, or do they?

“Black-boxes”: input and output impedances

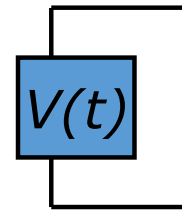- Consider a real voltage source, such as a transducer for temperature, e.g. a thermocouple:




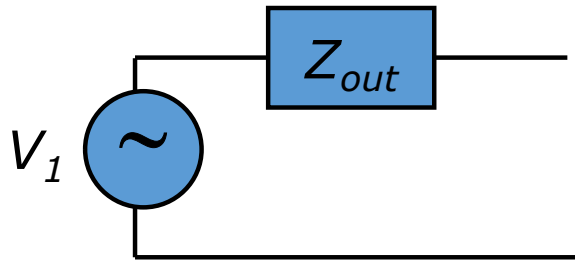- This can (Thevenin's theorem) always (in the linear regime) be represented by an equivalent circuit:



Here V_1 is a “perfect” voltage source – it can deliver an infinite current with V_1 constant – in series with an impedance.

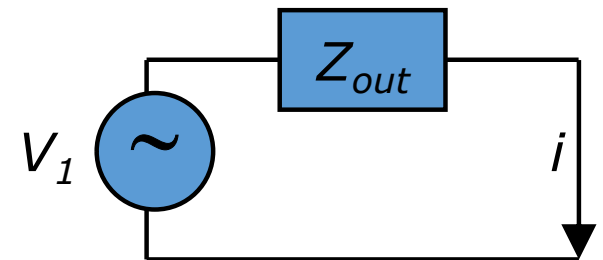- If the output is shorted, a current i flows (which we can measure with an ammeter).




- The output impedance of the transducer is defined as: $Z_{out} = V_1/i$.


Now consider connecting the transducer to a 'scope

- The oscilloscope's equivalent circuit is:

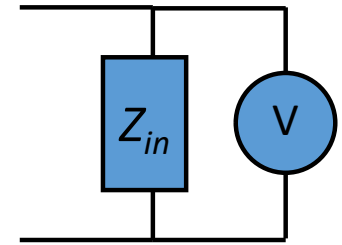It just consists of an impedance, the "input impedance" + ideal Voltmeter (which draws no current)



- So we have:

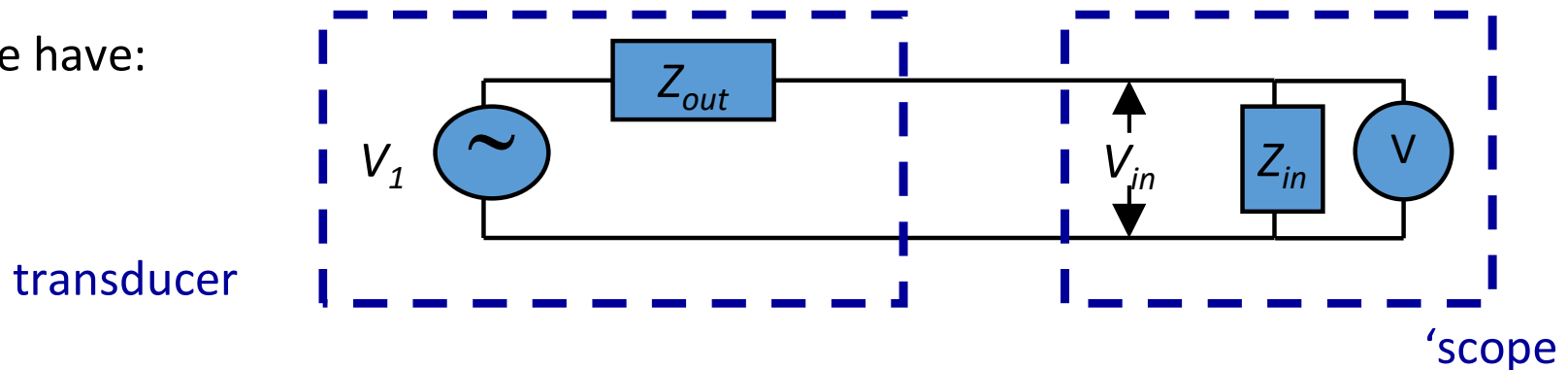

- Current conservation and Ohm's law \Rightarrow

$$\text{current in } Z_{out} = \text{current in } Z_{in} \Rightarrow \frac{V_1 - V_{in}}{Z_{out}} = \frac{V_{in} - 0}{Z_{in}}.$$

$$\text{So } V_{in} = V_1 \frac{Z_{in}}{Z_{in} + Z_{out}}.$$

So for measurements with a real transducer and a real oscilloscope we find

- The voltage measured by the 'scope \neq the voltage produced by the transducer.

$$V_{in} = V_1 \frac{Z_{in}}{Z_{in} + Z_{out}}$$


- For measurements to be approximately correct we need
 - Z_{in} very high – so the 'scope draws very little current.
 - Z_{out} very low – so the transducer provides as much current as possible.

Key insights

- It's easy to measure the wrong thing.
- This impacts both the transducer design and the measurement apparatus.
- For voltage measurements, we'd like:
 - A transducer with a low output impedance.
 - A measurement device with a high input impedance.
 - Typical 'scopes have Z_{in} at DC of 1-10 M Ω .

A second look at our measurement example

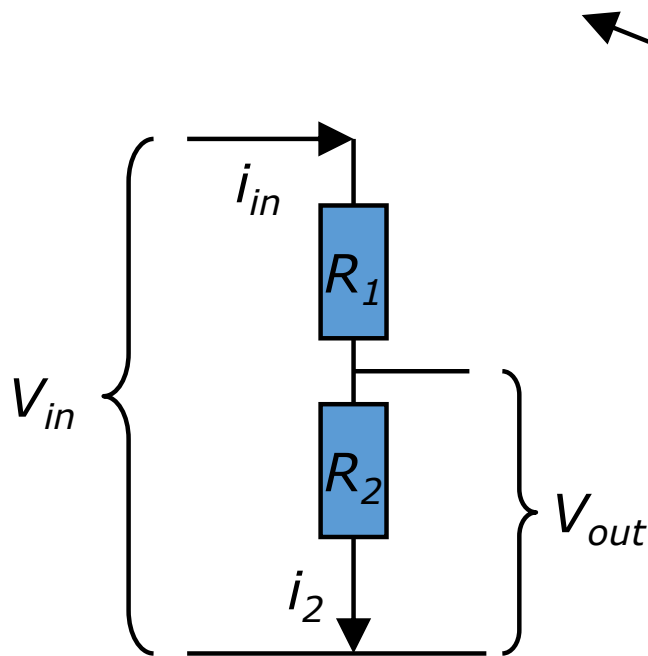- Consider a perfect resistor network with R_1 and R_2 , and a perfect measuring instrument.



This means the device measuring V_{out} has $Z_{in} = \infty$ so it takes no current.

$$\text{So, } i_{in} = \frac{V_{in}}{R_1 + R_2} = i_2 = \frac{V_{out}}{R_2}.$$

This is called a “potential divider”

$$V_{out} = V_{in} \cdot \frac{R_2}{R_1 + R_2} = V_{in} \times \frac{\text{resistance across } V_{out}}{\text{resistance across } V_{in}}.$$

What if the 'scope impedance is complex?


- In real 'scopes Z_{in} is complex.

- $R_{in} \sim 1M\Omega, C_{in} \sim 20pF$
- Assume our transducer has $R_{out} \sim 100\Omega$


$$Z_{in} = \left(\frac{1}{R_{in}} + i\omega C_{in} \right)^{-1} = \frac{R_{in}}{1 + i\omega C_{in} R_{in}}$$

$$Z_{total} = R_{out} + Z_{in}$$

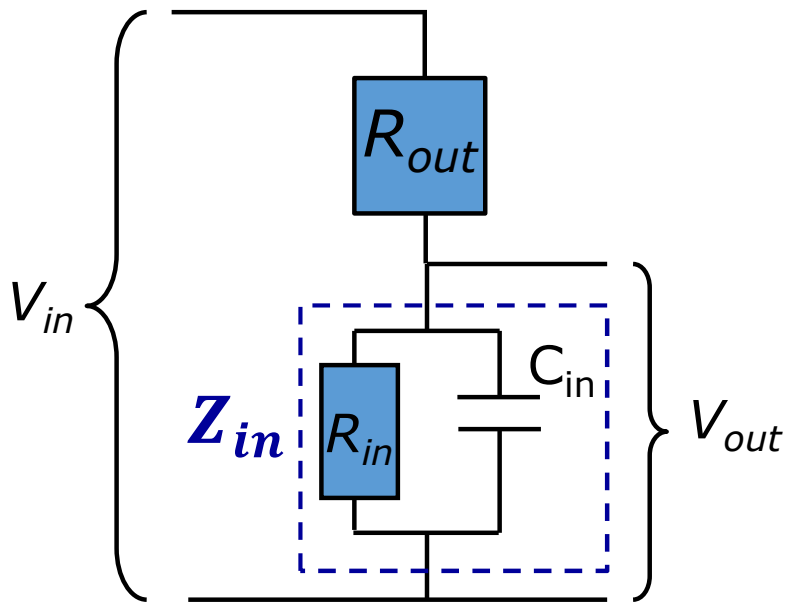
$$V_{out} = V_{in} \frac{Z_{in}}{Z_{total}}$$



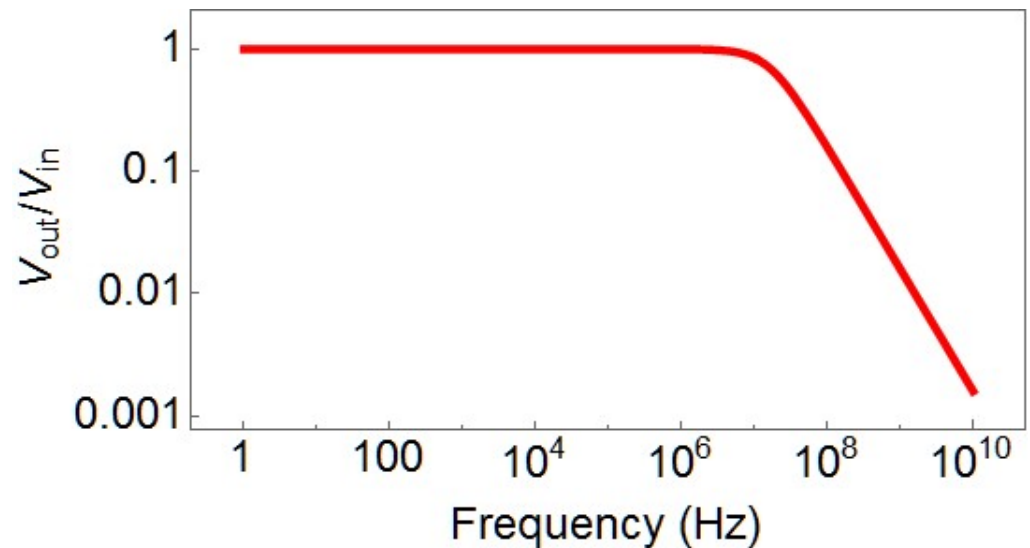
$$V_{out} = V_{in} \frac{\frac{R_{in}}{1 + i\omega C_{in} R_{in}}}{R_{out} + \frac{R_{in}}{1 + i\omega C_{in} R_{in}}} = V_{in} \frac{R_{in}}{R_{in} + R_{out}(1 + i\omega C_{in} R_{in})}$$



Can we fix this?

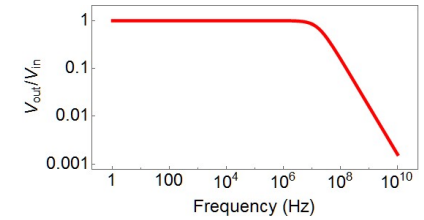

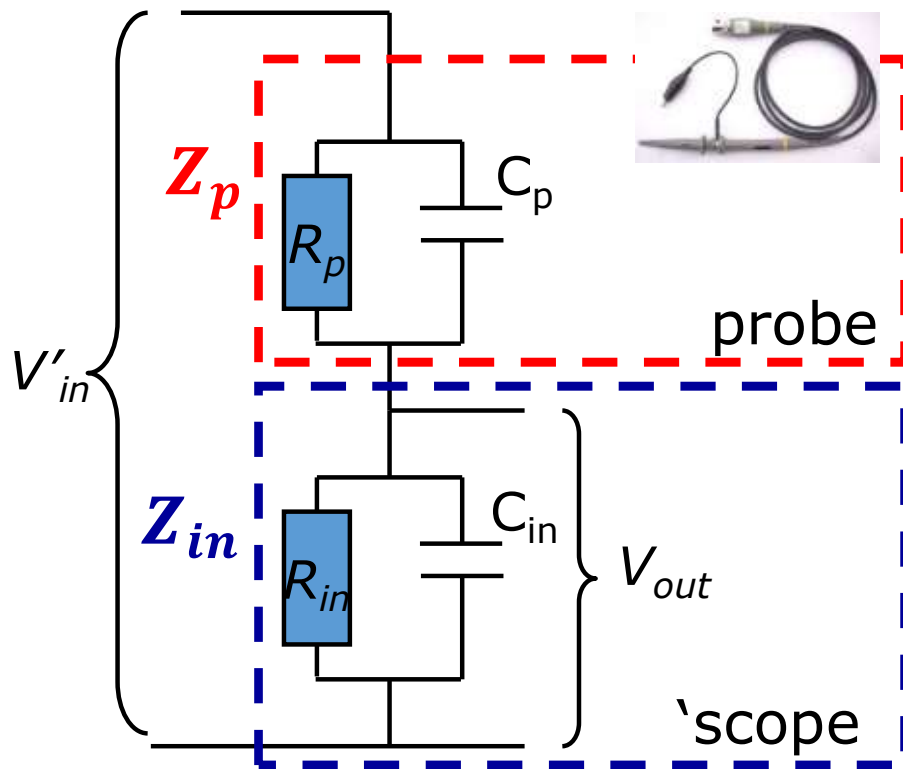This is a problem at high frequencies, but we can compensate **to some extent** using 'scope probes:



$$Z_{total} = Z_p + Z_{in}$$

$$V_{out} = V'_{in} \frac{Z_{in}}{Z_p + Z_{in}}$$

$$V_{out} = V'_{in} \frac{\frac{R_{in}}{1 + i\omega C_{in}R_{in}}}{\frac{R_p}{1 + i\omega C_p R_p} + \frac{R_{in}}{1 + i\omega C_{in}R_{in}}}$$

$$\text{If } C_{in}R_{in} = C_pR_p, \quad V_{out} = \frac{V'_{in} R_{in}}{R_{in} + R_p}$$

C_{in} is 'compensated', however $V_{out} \neq V'_{in}$

Some warnings regarding measurement


1. For current measurement, you least disturb the system if the measurement device takes all of the current – low Z_{in} .
2. To transfer maximum power from one system to another – (this is not equivalent to a non-invasive measurement) – then Z_{out} of one system must equal Z_{in} of the next:
 - ❑ EM radiation flux into a solar cell.
 - ❑ The gel used when having an ultrasound scan.(Impedance: ratio of a “potential” to a “flow”)

The high Z_{in} of a 'scope is great for measuring voltage signals, but little power gets into the oscilloscope.

In general, we frequently amplify and/or modify them:
Operational amplifier...

Operational Amplifiers – background



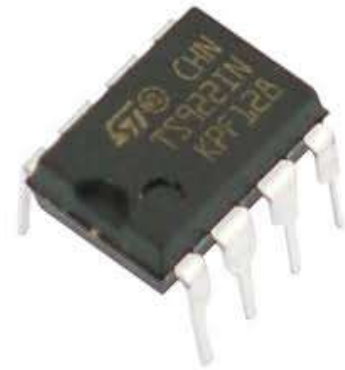
- Packaged, high gain, high input impedance **voltage** amplifiers:
 - Contain 10-100 transistors, Rs, Cs etc.
 - Contain very clever circuitry. [**we are skipping the electronics of discrete transistors!**]
 - Draw energy from a power supply.
 - You – as physicists – need to know **NONE** of the details



□ Why is this?

- We wish to use op-amps (not design them).
- In this case we can follow a “systems” approach and assume their behavior is characterized by a small number of properties.
 - This is what physicists routinely do when modelling the real world
 - It's also to some extent necessary (and common) to use equipment where we “trust” previous design/implementation.
- A real op-amp is a good approximation to an ideal amplifier (we will explore how good later).

How to 'view' an op-amp

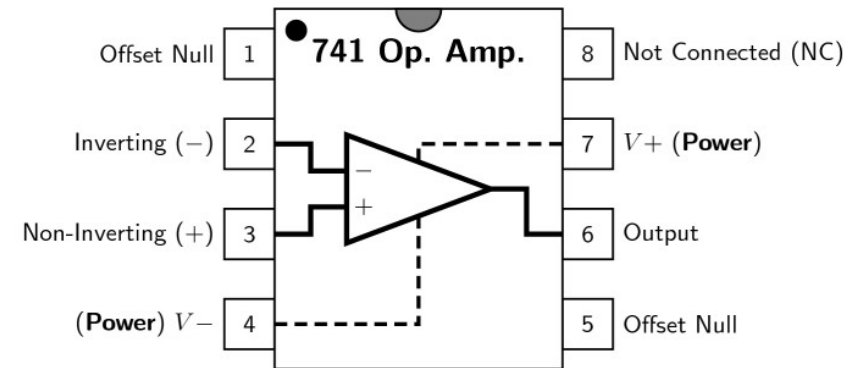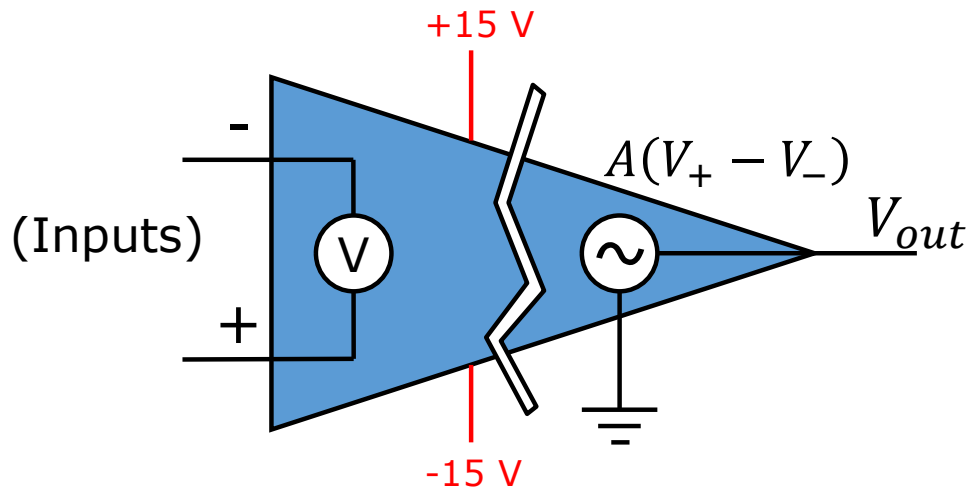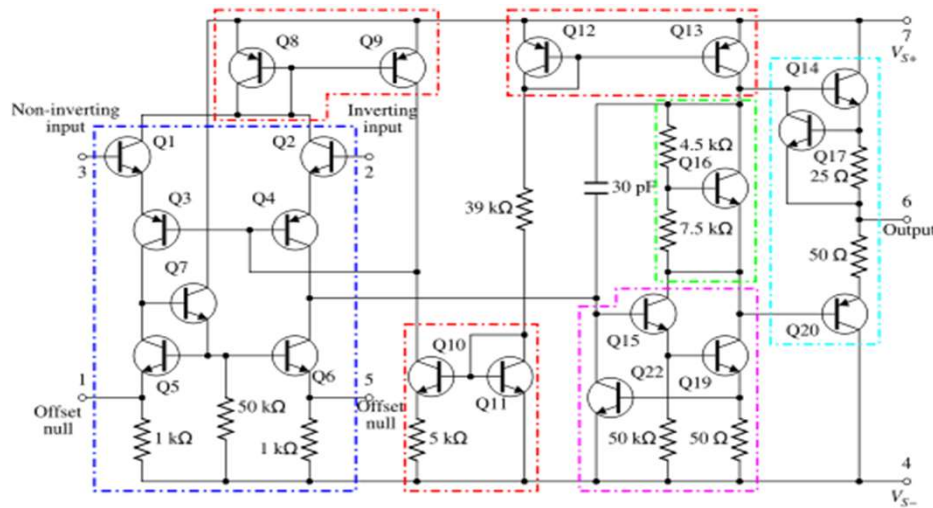

- Amplifier has an “open loop gain” of A

$$V_{out} = A(V_+ - V_-)$$

- So, for example, if we connect “+” input to a potential V_{in} and connect “-” input to ground:

$$V_{out} = AV_{in}$$

Properties of a model “ideal” voltage amplifier [\[assume these from now ... until we do otherwise!\]](#)

$$A = \infty$$


(in reality $A \gg 10^5$)

$$Z_{in} \equiv \frac{\partial V_{in}}{\partial i_{in}} = \infty$$

If the amplifier is fed with a small current that doesn't matter.

$$Z_{out} \equiv \frac{\partial V_{out}}{\partial i_{out}} = 0$$

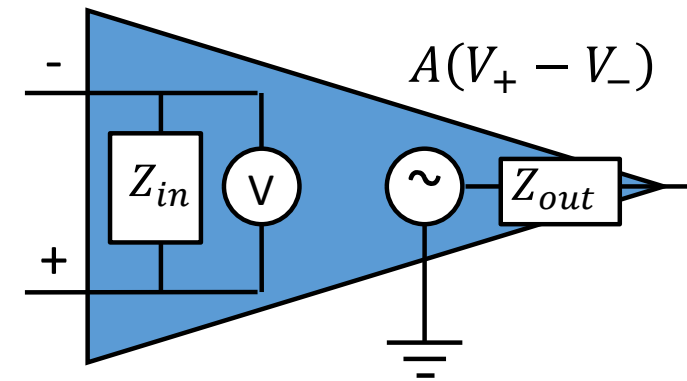So it can provide lots of current to what it is connected to.



Let's ask ourselves: would such an ideal amplifier be useful?

If $A = \infty$, even a tiny V_{in} would make $V_{out} = \infty$

(or rather equal to the $\pm 15V$ supply limit...)

We can make such an infinite gain amplifier useful by using “negative feedback”


$$V_{out} = A(V_+ - V_-)$$

- We sense a fraction of the output and connect to the –ve input.
- As the output rises, the amplifier starts lowering it.
- An equilibrium is reached that stops the output saturating
 - Under these circumstances, the analysis of circuits involving such amplifiers is relatively straightforward.

GOLDEN RULES FOR ANALYSING IDEAL OP-AMPS

- Golden Rule #1: the inputs draw no current:
 - Because Z_{in} is infinite.
- Golden Rule #2: The voltages on the “+” and “-” inputs are the same, unless the output is saturated:
 - Because A is so high, if the output is not to saturate, the voltages at the “+” and “-” inputs must be *very close* to equal.
 - Note: one must provide *negative feedback* to achieve this.

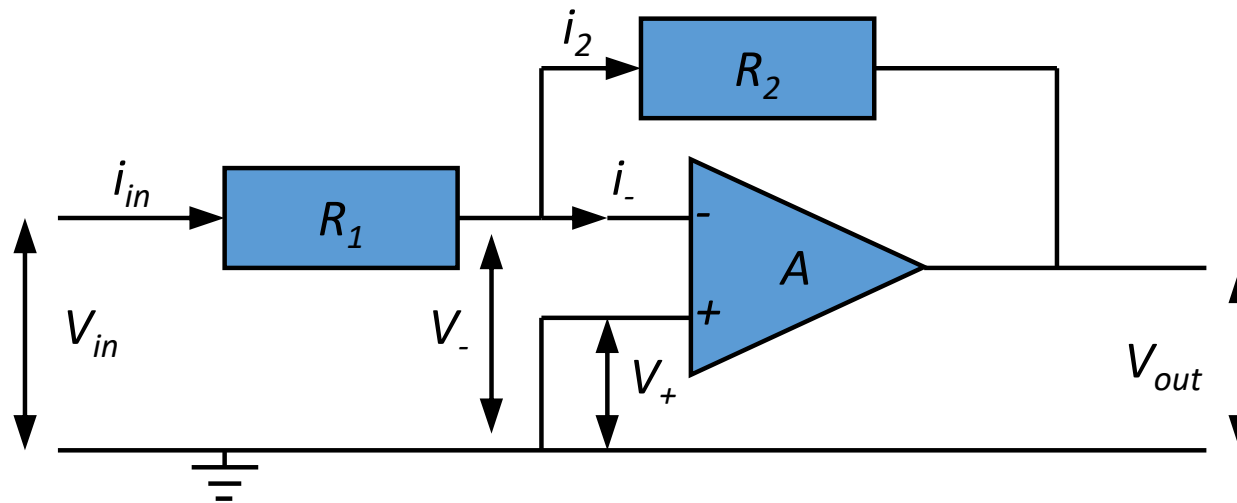How to wire up an inverting voltage amplifier



- Want to find the self-consistent solution for V_{out}/V_{in} .
- This is called the “closed-loop” gain, i.e. the gain of the circuit with feedback.

□ Step 1:

- $V_+ = 0$. So GR2 $\Rightarrow V_- = 0$.
- In this situation, the “-” pin is called a “virtual earth”.


Step 2: conserve current and use Ohm's law

- **GR1** $\Rightarrow i_- = 0$. So, $i_{in} = i_2$.

$$\left. \begin{aligned} i_{in} &= \frac{V_{in} - \cancel{V_-}}{R_1} \\ i_2 &= \frac{\cancel{V_-} - V_{out}}{R_2} \end{aligned} \right\} \quad (= 0)$$

$$\text{gain} \equiv \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$

i.e, independent of A

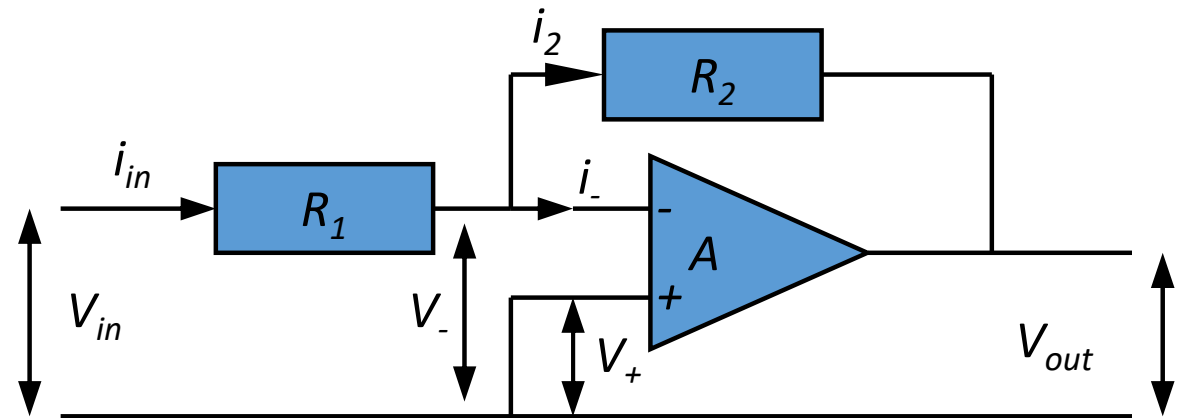

- Remember to apply a p.d. sign convention consistently. Here we have taken V_{in} as highest, V_- less, and V_{out} least (hence the current flow directions). Can, e.g., reverse this but the solution will be the same.

So, what does this mean in practice?

- Provided the op-amp is ideal (or nearly so):
 - We can use the systems approach.
 - The gain of the **circuit** is set by **just the two resistors**.
 - With negative feedback present at all frequencies, circuit will amplify provided V_{in} is not so high that V_{out} reaches ± 15 V.

Skipping in lecture today

Can we better justify golden rule 2 ($V_+ = V_-$)?

- What if we don't assume it's true? Remember A is very large ($> 10^5$)

Since V_+ is grounded, the op-amp output:

$$V_{out} = A(V_+ - V_-) = -AV_-$$

Ohm's Law across R_1 and R_2 :


$$i_{in} = \frac{V_{in} - V_-}{R_1}, \quad i_2 = \frac{V_- - V_{out}}{R_2}$$

GR1 ($i_- = 0$), so conserving current:

$$i_{in} = i_2 = \frac{V_{in} - V_-}{R_1} = \frac{V_- - V_{out}}{R_2}$$

$$V_{out} = -\frac{R_2}{R_1}V_{in} + \left(1 + \frac{R_2}{R_1}\right)V_-$$
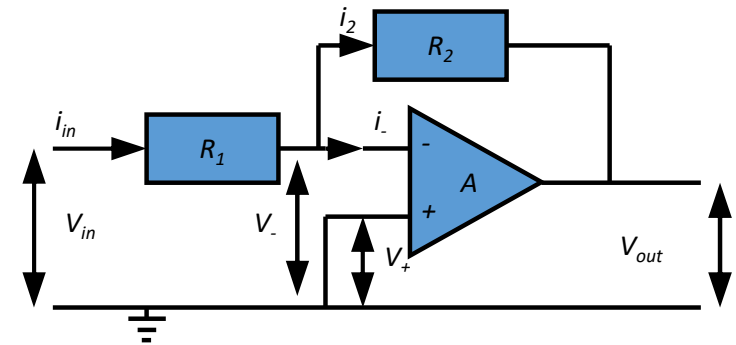
$$V_{out} = -\frac{R_2}{R_1}V_{in} - \left(1 + \frac{R_2}{R_1}\right)\frac{V_{out}}{A}$$



$$V_{out} = -\frac{R_2}{R_1}V_{in} \left(\frac{A}{A + \left(1 + \frac{R_2}{R_1}\right)} \right) \approx -\frac{R_2}{R_1}V_{in}$$

$$V_+ - V_- \approx -\frac{1}{A} \frac{R_2}{R_1} V_{in} \approx 0$$

(a very small number!)


Golden Rule 2!

So feedback + large $A \rightarrow$ GR2

We can also wire non-inverting amplifier circuits

- Step 1:

- GR2 $\Rightarrow V_- = V_+ = V_{in}$

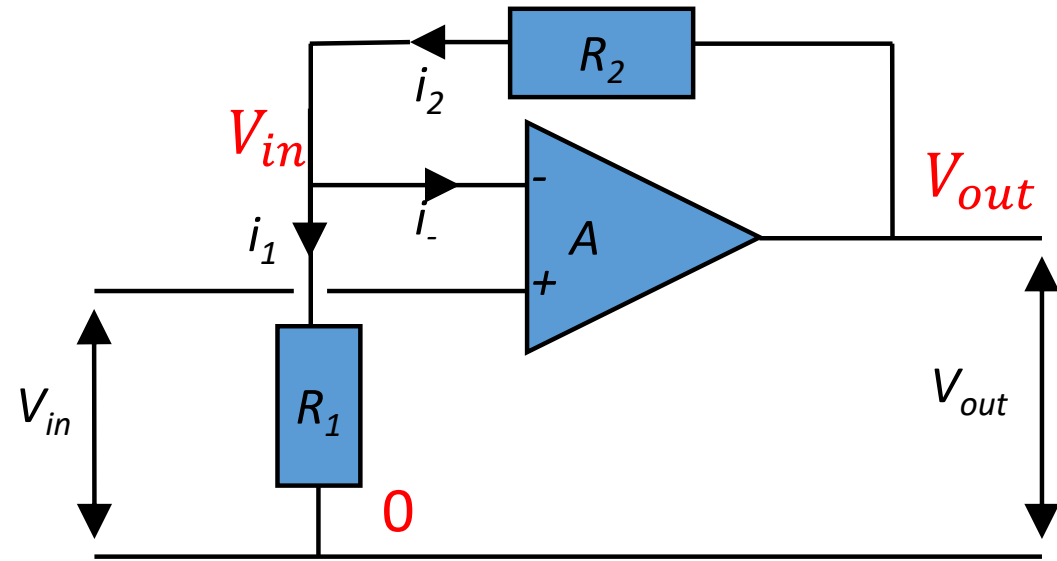


- Step 2: conserve currents and use Ohm's law and GR1

$$i_2 = i_1 + i_- \Rightarrow \frac{V_{out} - \overset{= V_{in}}{V_-}}{R_2} = \frac{V_- - 0}{R_1} + 0$$

$$\Rightarrow \text{gain} \equiv \frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}$$

We can understand the non-inverting circuit in a different (and helpful) way

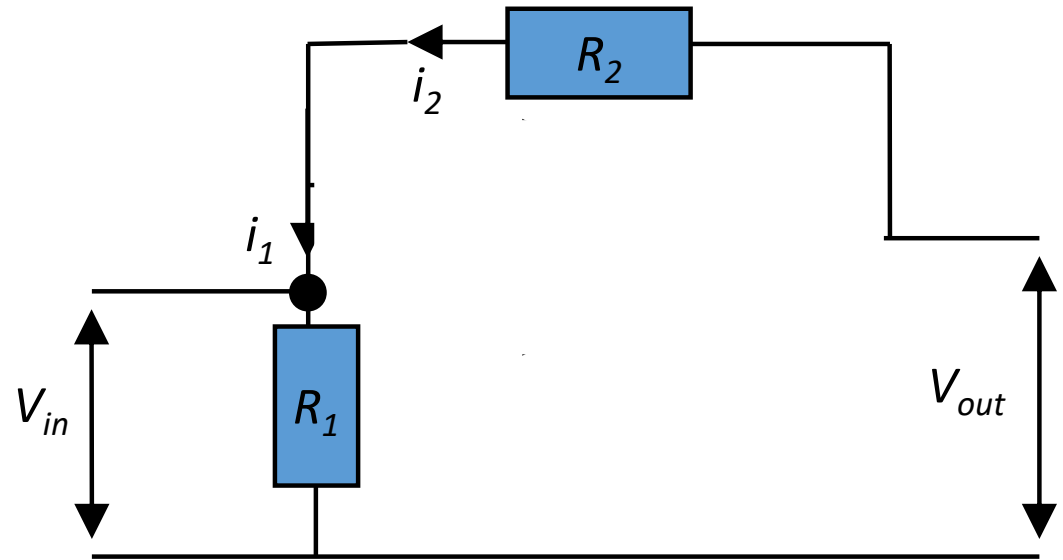- **GR1** $\Rightarrow i_- = 0$ & **GR2** $\Rightarrow V_- = V_+ = V_{in}$ (as before)



□ Can recognize that:



- R_1 and R_2 are acting as a potential divider across V_{out} and ground (i.e. 0V)

$$V_- = V_{in} = \frac{R_1}{R_1 + R_2} \cdot V_{out} \Rightarrow \frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}.$$

- Recovering our previous result.

Op-amps can be used to do much more than make amplifiers...

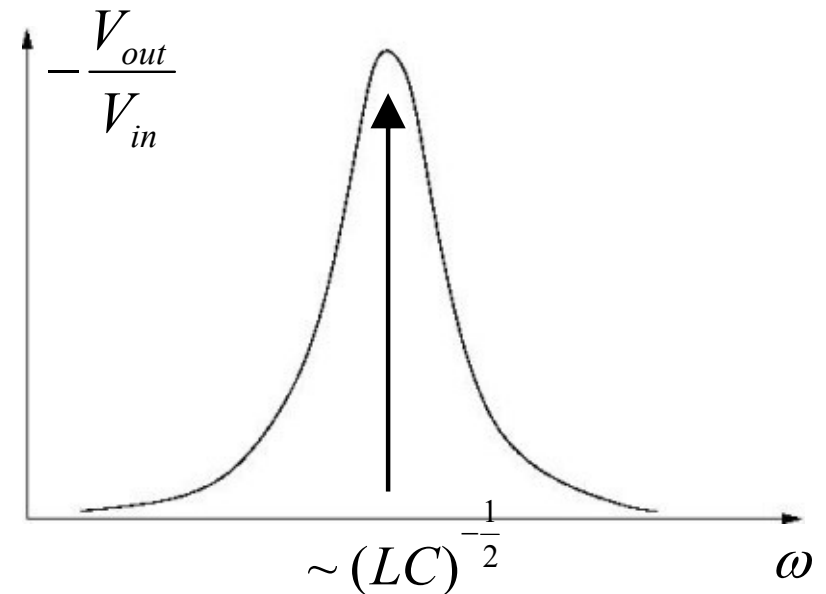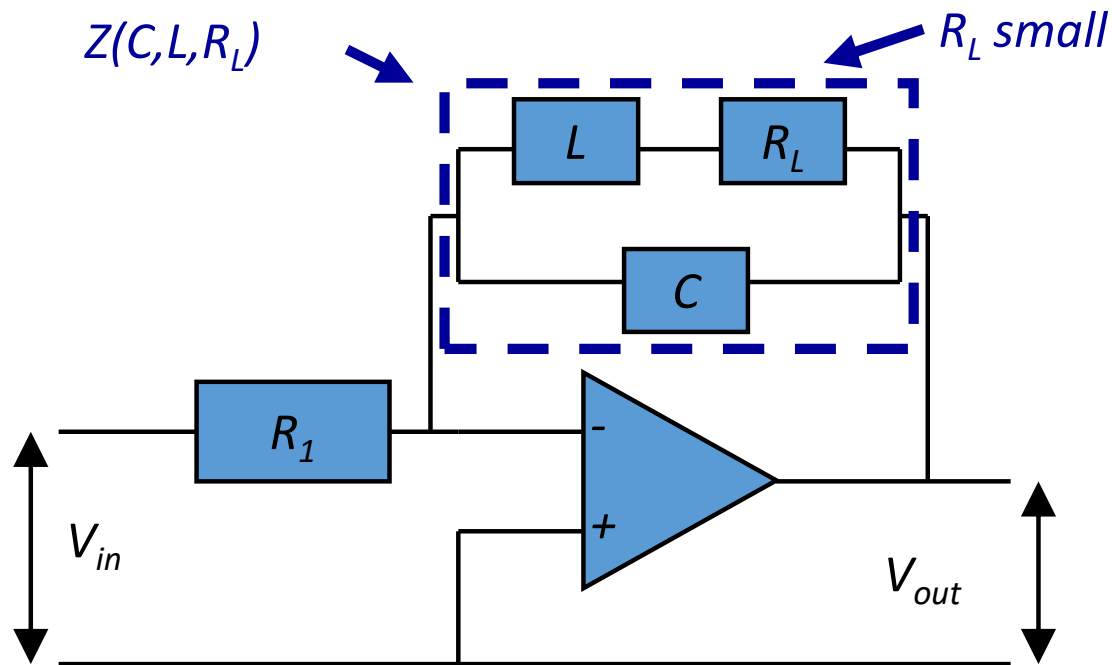- The external components don't have to be just resistors – can be R_s , C_s , L_s and more
 \Rightarrow e.g. integrators, differentiators, filters...



- This is useful for amplifying signals close to a wanted frequency and filtering out the rest.

Summary so far

- Making a measurement very likely may \Rightarrow measuring a small electrical signal.
- This must be measured faithfully, and possibly amplified and filtered.
- If we have an ideal high gain voltage amplifier we now know how to use it in a circuit.
- The circuit gain ($=V_{out}/V_{in}$) can be set by a few external components as long as they are arranged to give negative feedback.

Considering non-ideal performance

- How does non-ideal op-amp behaviour affect our previous results and their use in the lab:
 - Modelling non-ideal behavior.
 - Gain, Z_{in} , Z_{out} ?
- How do we manage other “failings” when measuring with a real device:
 - For example, frequency response.

What do we mean by a non-ideal op-amp?

A not ∞ but 10^4 – 10^6 .

Z_{in} not ∞ but high, and Z_{out} not 0 but low.

A is complex and a function of frequency.


The amplifying circuitry has a finite slew rate, dV_{out}/dt .

There is an input “bias current” independent of V_{in} (10^{-12} – 10^{-7} A) that sets an upper limit to external resistor values.

There is an output voltage independent of $(V_+ - V_-)$ – equivalent to a differential offset of 10^{-3} to 10^{-2} V – that must be balanced with an external potentiometer.

Annoying but not show-stoppers

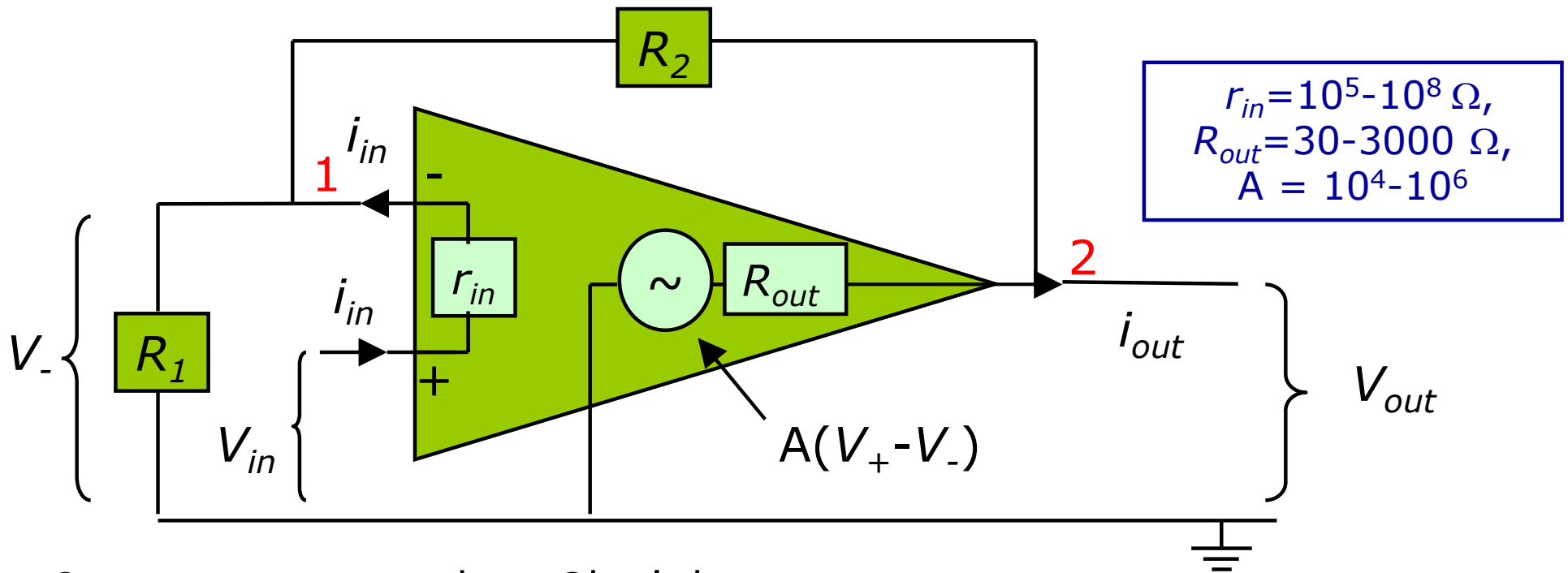
A reasonable more realistic model for the non-inverting case



□ Conserve current and use Ohm's law:

■ At 1:
$$i_{in} = \frac{V_{in} - V_-}{r_{in}} = \frac{V_- - 0}{R_1} + \frac{V_- - V_{out}}{R_2}$$

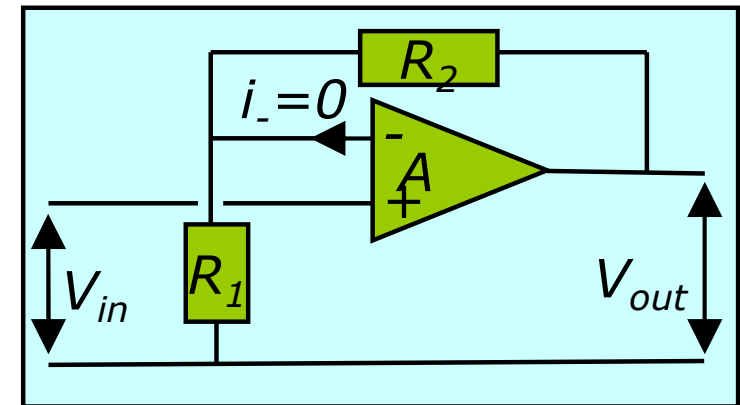■ At 2:
$$i_{out} = \frac{A(V_{in} - V_-) - V_{out}}{R_{out}} + \frac{V_- - V_{out}}{R_2}$$




What we do now is eliminate the unknowns to get the characteristics of the **circuit**

- We treat the whole **circuit** as a “system” with an effective input impedance, an open-loop gain, and an output impedance such that we can write

$$V_{out} = V_{in} \cdot (\text{open loop gain}) - i_{out} \cdot (\text{output impedance})$$

(G) (Z_{out})

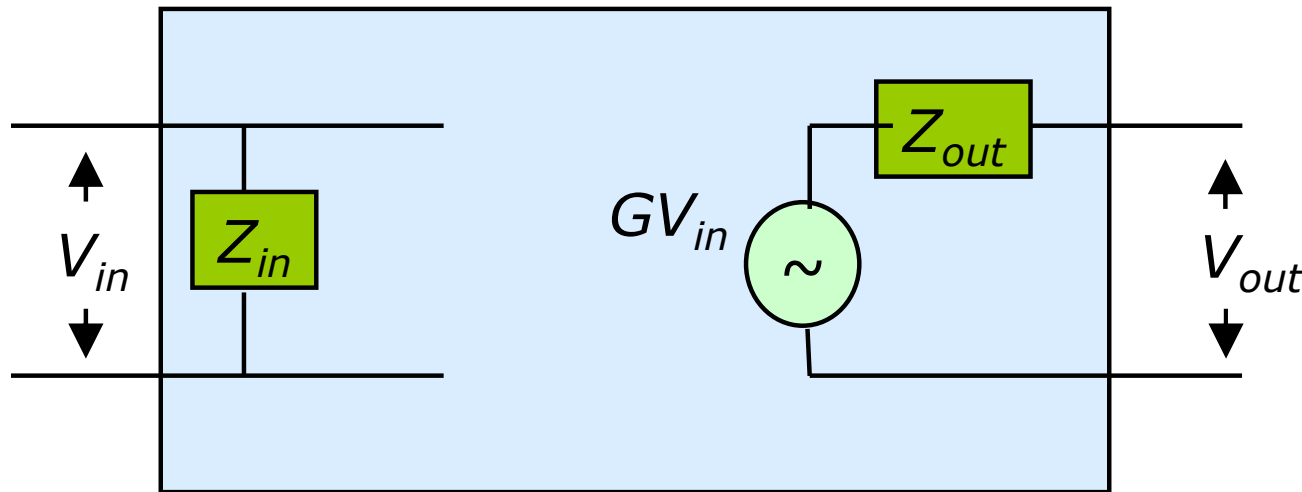

- We hope Z_{in} of the “system” is high and Z_{out} for the “system” is low.

Let's do the algebra, how does this “model” **circuit** compare to our “perfect” op-amp?

- For large A and large r_{in} :

$$V_{out}/V_{in} = 1 + \frac{R_2}{R_1}$$

$$A = 10^4 - 10^6, \\ r_{in} = 10^5 - 10^8 \Omega, R_{out} = 30 - 3000 \Omega$$

- As in the ideal case, like the Golden rules.

- For large A and large r_{in} :

$$Z_{out} \rightarrow \frac{R_{out}}{A} \left(1 + \frac{R_2}{R_1} \right)$$

- So the **circuit** has a lower Z_{out} than R_{out} of the op-amp itself.

- For large A and low R_{out} :

$$Z_{in} \rightarrow \frac{r_{in} A}{1 + R_2/R_1}$$


- So the **circuit** has a higher Z_{in} than r_{in} of the op-amp itself. This amplifying circuit can have a $Z_{in} \sim 10^{12} \Omega$.

So basically if A is big, in this configuration the performance of the circuit as a voltage amplifier is almost “perfect”

This is because we have negative feedback – it’s the crucial aspect of the circuit.


- A useful, though apparently extreme, case of a non inverting amplifier has $R_2/R_1=0$:

The “buffer” or “follower”

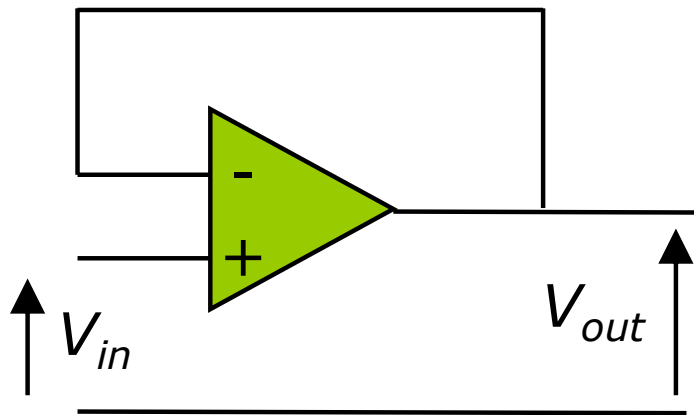

$$V_{in} = V_{out}$$

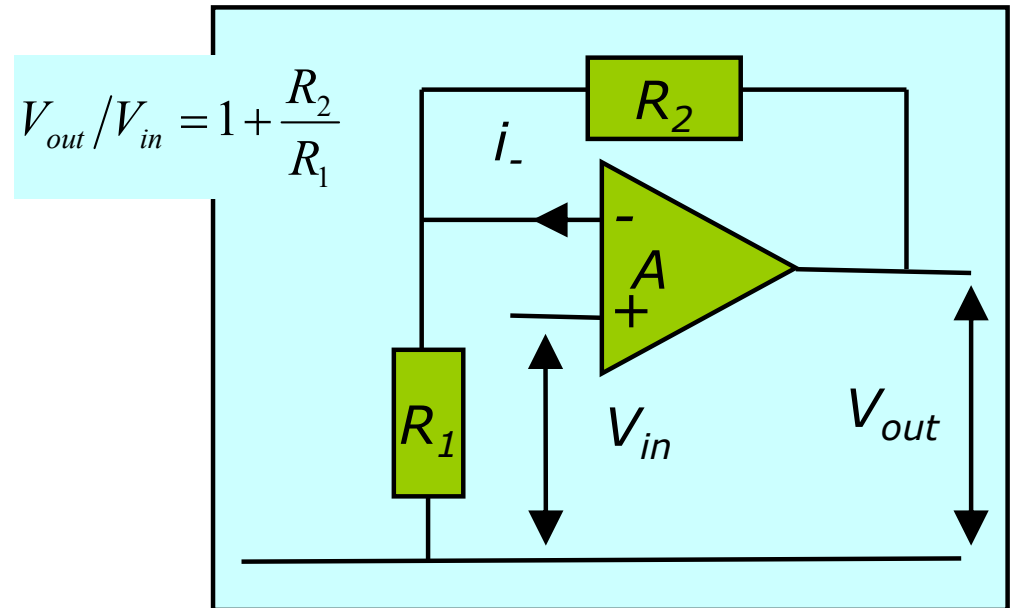
$$\text{BUT: } Z_{in} = r_{in} \cdot A \quad \text{and} \quad Z_{out} = \frac{R_{out}}{A}$$



$$V_{out}/V_{in} = 1 + \frac{R_2}{R_1}$$

Use this to “connect” two circuits together

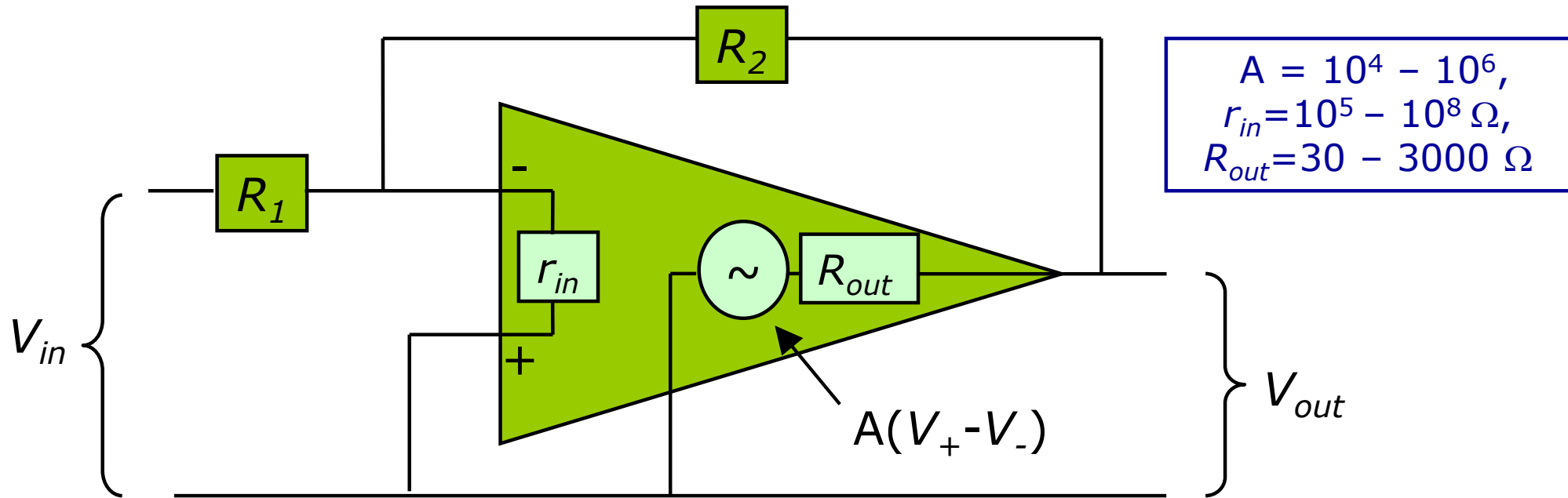We can similarly model the inverting non-ideal amplifier configuration




- Again, don't analyze with the Golden Rules, but just conserve current and use Ohm's law.

We find, provided A is high:

$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$


As in the ideal case again.

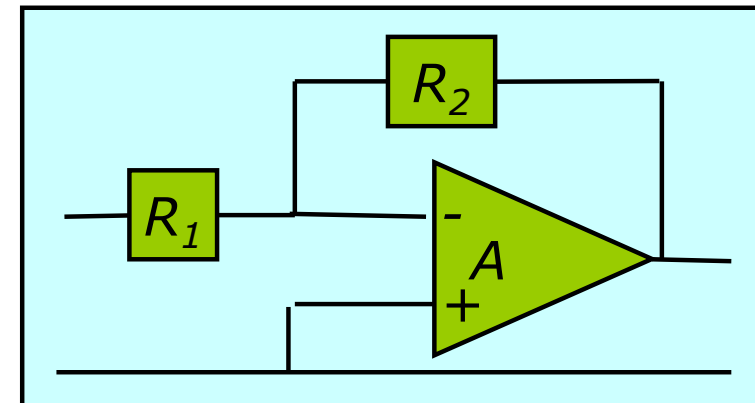

Similarly, we can solve for the input and output impedances of this circuit. Are Z_{in} high & Z_{out} low?

□
$$Z_{out} = \frac{R_{out}}{A} f\left(\frac{R_2}{R_1}\right)$$
 Good – with a typical op amp and $R_1=1k$ and $R_2=10k$, $Z_{out} = 10^{-3} \Omega$

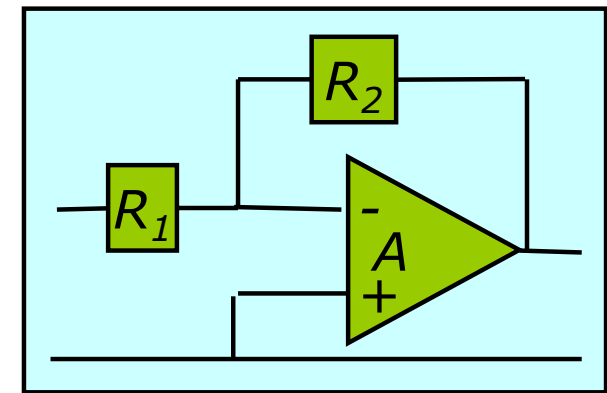
□ But...
$$Z_{in} = R_1 + \text{low - valued } f\left(\frac{R_1, R_2, r_{in}}{A}\right)$$
 “virtual-earth” arrangement



- If R_1 is, say, 1k – then this is small compared with r_{in} (10^5 - $10^8 \Omega$), though large compared with Z_{out} ($\sim 10^{-3} \Omega$) of a previous op-amp stage.
- If you really need Z_{in} high, then use a non-inverting system.


Other shortcomings: frequency dependence

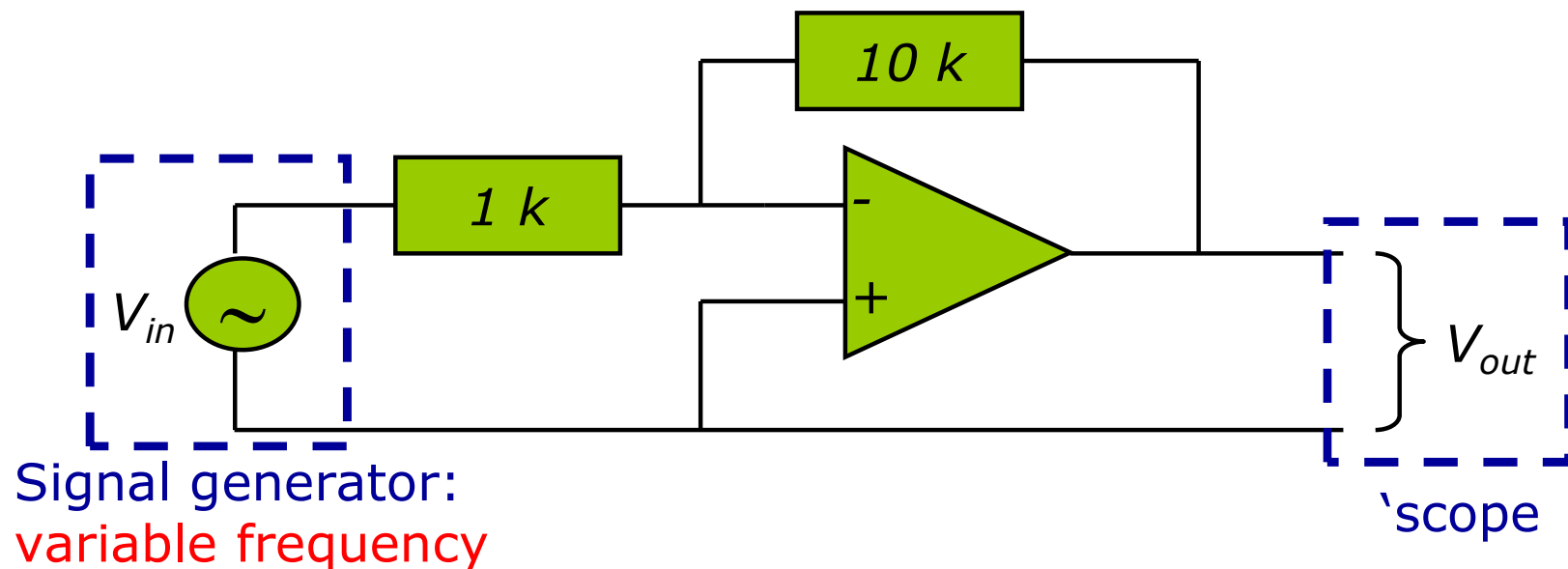- Most measurements involve a range of frequencies:
 - Seismic waves 0.1 Hz – 10 Hz
 - LIGO 50 Hz – 1 kHz
 - Human hearing 20 Hz – 20 kHz
 - Ultrasound 50 kHz – 200 kHz
- In the practical lab you might explore the frequency response of a typical op-amp circuit by [measuring](#) it with a set up with a nominal gain of 10.




The measured gain of the **circuit** implies that op-amps have a built in reduction of A – why?

- In general we find:

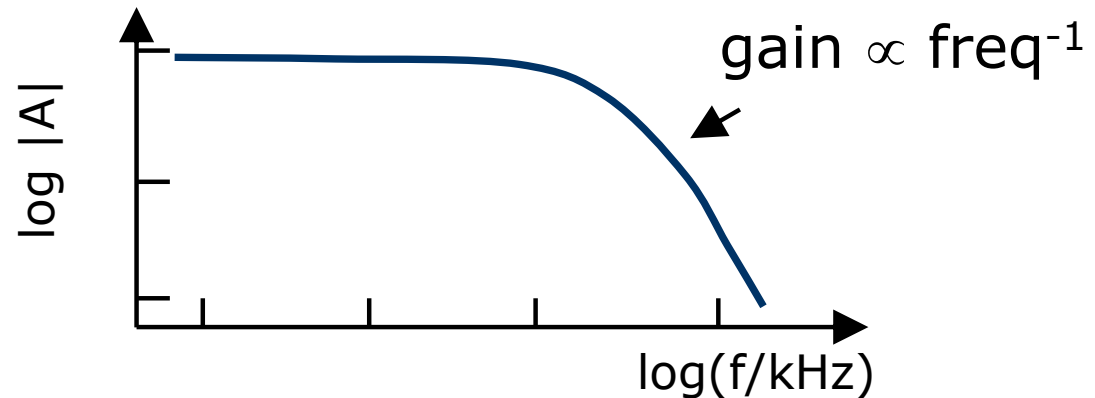

- Consider the feedback resistor, R_2 , in this circuit:

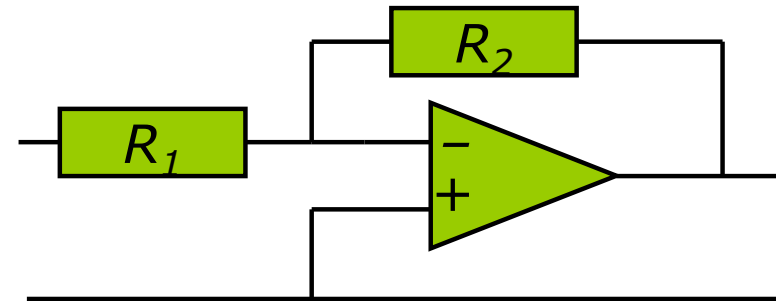- A real R_2 will actually be $Z(L, C, R, \omega)$, i.e. have a complex impedance






- So, over a big enough frequency range, this can lead to a phase shift of π . This will change $-ve$ feedback into $+ve$ feedback \Rightarrow saturation/oscillation rather than amplification.

Is this really important for low freq. circuits?

□ Consider switching a circuit on:

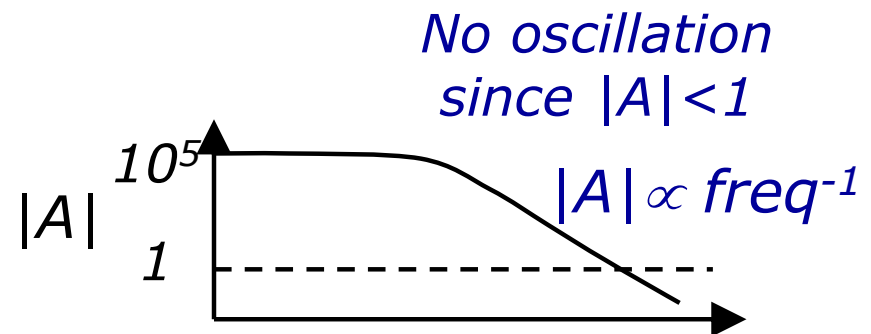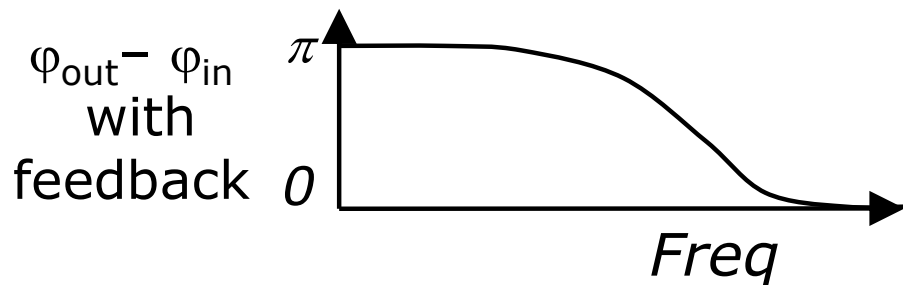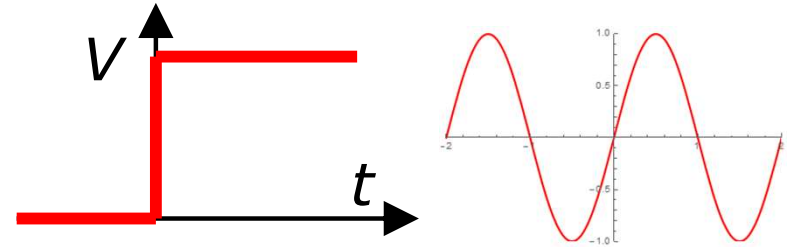- This step has Fourier components at all frequencies, so positive feedback is bound to happen.
- So, op-amps are designed to have “internal frequency compensation” so that A itself falls at high frequencies.



□ In itself, this is not always sufficient. Also need to stop oscillation-inducing signals getting back to the inputs, e.g.:

- Pick-up from stray EM radiation: screen.
- Along supply lines – use decoupling capacitors.

Summary

This one op-amp lecture is the bare minimum one needs to know about op-amps

It already allows you to build a vast number of useful circuits.